

2021
Computer Science (Honours)
2nd Semester Paper DC - 4(a)
Digital Logic System
[CBCS]

Full Marks: 25

Time: 2 hours

The figures in the margin indicate full marks.

Group -A

(2 x 5 = 10)

Answer any five questions.

1. a. Distinguish between mux and demux.
- b. What is Race around Condition?
- c. Draw a truth table for the equation given below:

$$Y = A (B + C + \bar{D}) + CD$$

- d. Reduce the given Boolean expression.

$$Y = A\bar{B}C (BD + CDE) + A\bar{C}$$

- e. Apply DeMorgan's theorem to the following expression.

$$\bar{B} (D + BDE) + ABC$$

- f. What is priority encoder?

Group -B

(5 X 3 = 15)

Answer any three questions.

2. Design an adder/ subtractor circuit that performs addition/ subtraction depending on the user's choice. Explain it briefly.
3. Design a Master Slave J-K Flip Flop using NAND gates only.
4. What is full subtractor? Realize a full adder circuit using a 3 x 8 decoder. 1+4=5
5. Design a Mod-5 Counter and explain it briefly.
6. Using the K-map method, obtain the minimal sum of product expression of the following function.

$$Y = \sum (0, 2, 3, 6, 7, 8, 10, 11, 12, 15) + d (5, 9, 13)$$

2+3=5